

Computer-Aided Design for VLSI Design

Homework2 (Student ID: 61047046S | Name: 鄭琮達)

1. Provide a simple explanation of your code.

在作業中我使用到 `use ieee.std_logic_unsigned.all;` 來幫我解決”+”只能用在整

數的問題，在 structural model 使用 component 語法合併我的 D-FF 以及

Adder。以下為我的 code 以及 RTL Viewer

(a) Behavior Model

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;
```

```
entity My_count is
```

```
port(  
    clk: in std_logic;  
    Q: out std_logic_vector(7 downto 0));
```

```
end My_count;
```

```
architecture behavior of My_count is
```

```
    signal Q_in: std_logic_vector(7 downto 0) := "00000000";
```

```
begin
```

```
    process(clk)
```

```
    begin
```

```
        if(clk'EVENT and clk='1') then
```


```
            Q_in <= Q_in + "011";
```

```
        end if;
```

```
    end process;
```

```
    Q <= Q_in;
```

```
end behavior;
```

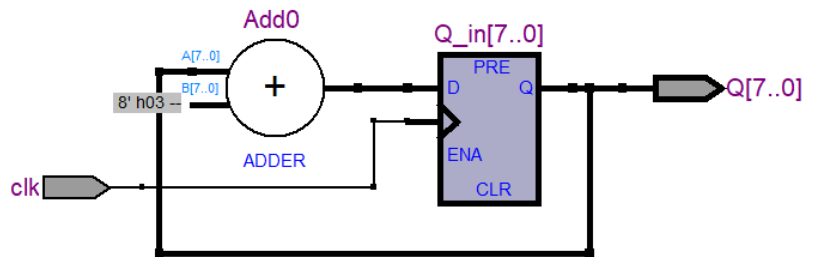

(b) Structural Model

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;


entity My_struct_count is
port(
    clk: in std_logic;
    Q: out std_logic_vector(7 downto 0));
end My_struct_count;

architecture structural of My_struct_count is
    component My_DFF
    port(
        clk: in std_logic;
        Q_in: in std_logic_vector(7 downto 0);
        Q_out: out std_logic_vector(7 downto 0)
    );
    end component;

    component counter
    port(
        add_A: in std_logic_vector(7 downto 0);
        add_B: in std_logic_vector(7 downto 0);
        sum : out std_logic_vector(7 downto 0)
    );
    end component;

    signal Q_in, Q_out : std_logic_vector(7 downto 0);
    constant B : std_logic_vector(7 downto 0) := "00000011";
begin
    C1: My_DFF port map(clk, Q_in, Q_out);
    C2: counter port map(Q_out, B, Q_in);
    Q <= Q_out;
end structural;

```

 

```

library ieee;
use ieee.std_logic_1164.all;

entity My_DFF is
port(
    clk: in std_logic;
    Q_in: in std_logic_vector(7 downto 0);
    Q_out: out std_logic_vector(7 downto 0));
end My_DFF;

architecture behavior of My_DFF is
begin
    process(clk)
    begin
        if(clk'EVENT and clk='1') then
            Q_out <= Q_in;
        end if;
    end process;
end behavior;

```

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;


entity counter is
port(
    add_A: in std_logic_vector(7 downto 0);
    add_B: in std_logic_vector(7 downto 0);
    sum : out std_logic_vector(7 downto 0));
end counter;

architecture behavior of counter is
begin
    process(add_A)
    begin
        sum <= add_A + add_B;
    end process;
end behavior;


```

2. Waveform diagram here (Simulation Results)

(a) Behavior Model

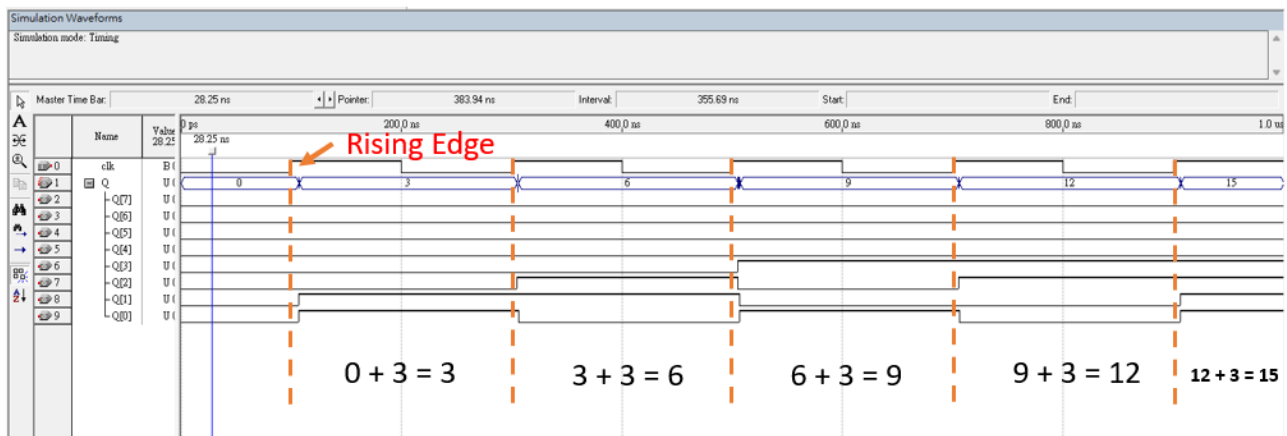

(b) Structural Model

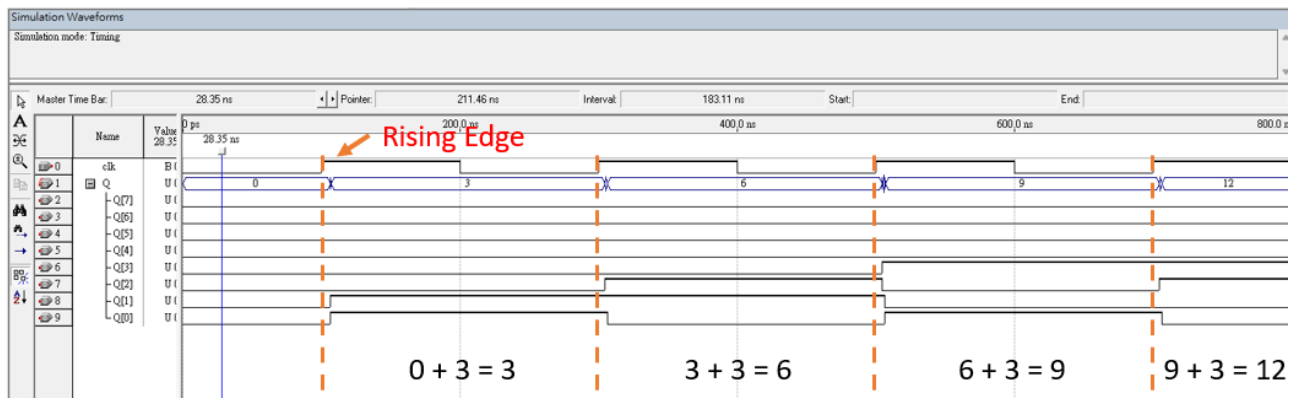

3. Reflections and discussions

謝謝教授以及助教提供作業讓我學習 behavior model 以及 structural model

的使用方式，透過 Rising Edge 的方法來設計加法器，在這份作業上，我學

會不僅可以+3，也可以使程式加特定的數字。以及利用教授課堂提醒到的

std_logic_unsigned 可以用來解決非整數加法運算的問題。